

**UNIVERSITY COLLEGE TATI (UC TATI)****FINAL EXAMINATION QUESTION BOOKLET**

COURSE CODE	: DEE 1113	311
COURSE	: ELECTRICAL TECHNOLOGY I	
SEMESTER / SESSION	: 02 - 2024/2025	
DURATION	: 3 HOURS	

**Instructions:**


1. This booklet contains **4** questions. Answer **ALL**.
2. All answers should be written in the answer booklet.
3. Write legibly and draw sketches wherever required.
4. If in doubt, raise your hand and ask the invigilator.

**DO NOT OPEN THIS BOOKLET UNTIL YOU ARE TOLD TO DO SO****THIS BOOKLET CONTAINS 9 PRINTED PAGES INCLUDING COVER PAGE**

**QUESTION 1**

- a) State the definition of electric charge. (2 marks)
- b) State the definition of electric current. (2 marks)
- c) State the definition of electric voltage. (2 marks)
- d) Determine the number of electrons needed to carry 250 mC of charge. (3 marks)
- e) Determine the amount of work (Joules) required to carry 6 coulombs of charge in a 12 V battery. (3 marks)
- f) Determine the battery voltage value when it takes 10 Joules to move 15 coulombs of charge through the conductor. (3 marks)
- g) Given bulb resistance of 300  $\Omega$  and current flow through is 100 mA. Find the power dissipated on the bulb. (3 marks)
- h) Find the current through a wire if 25 coulombs of charge flow past a given point in 2s. (3 marks)
- i) Determine the resistor color code for the following resistors. The tolerance is 10%.
- i. 12 k $\Omega$  (2 marks)
- ii. 4.7 M $\Omega$  (2 marks)
- j) Determine the expected value for the resistors with the following color codes.
- i. red/red/black/gold (2 marks)
- ii. grey/red/yellow/silver (2 marks)

- k) Calculate the total resistance,  $R_T$  based on **Figure 1** from point A to point B.

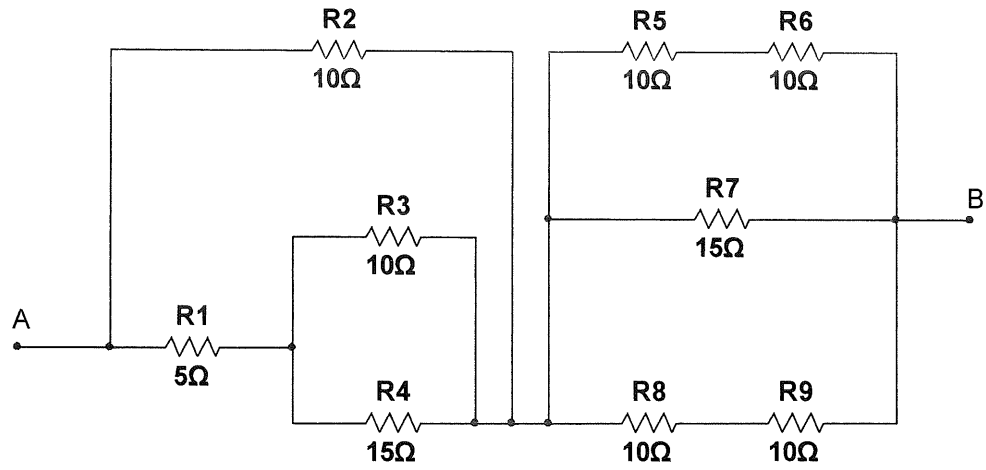


**Figure 1**

(6 marks)

**QUESTION 2**


- a) Describe the behaviour of current and voltage drop in a series circuit. (2 marks)
- b) Describe Kirchoff's Voltage Law (KVL). Support your answer with an illustration. (3 marks)
- c) Determine the voltage drop across resistors  $R_1$ ,  $R_2$  and  $R_3$  in **Figure 2**.

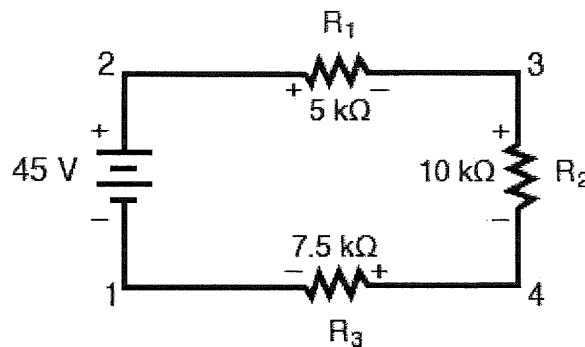

**Figure 2**

(6 marks)

- d) Describe the behaviour of current and voltage drop in a parallel circuit. (2 marks)
- e) **Figure 3** shows a parallel circuit.
  - i. Determine the total resistance,  $R_T$  of the circuit. (3 marks)
  - ii. Determine the total current,  $I_{total}$  flow through the circuit. (3 marks)
  - iii. Determine the current  $I_{R1}$ ,  $I_{R2}$  and  $I_{R3}$  flowing through resistors  $R_1$ ,  $R_2$  and  $R_3$ . (6 marks)

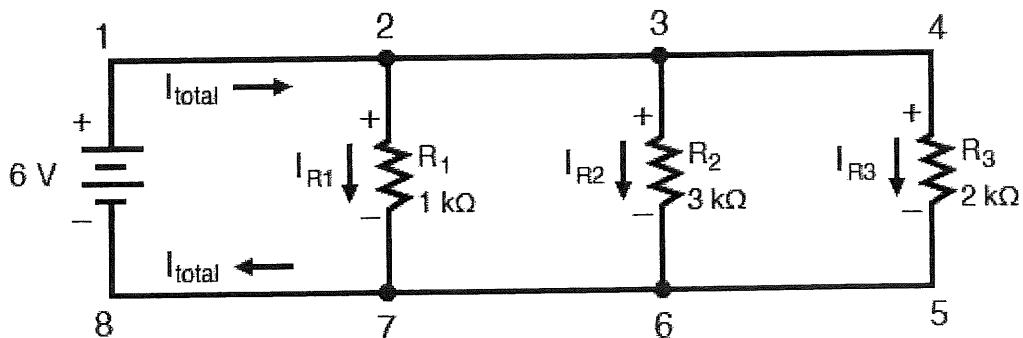

**Figure 3**

f) **Figure 4** shows resistors parallel to a current source.

- i. Calculate the current  $I_{R1}$ ,  $I_{R2}$  and  $I_{R3}$  flowing through resistors  $R_1$ ,  $R_2$  and  $R_3$ . Show all calculations. (8 marks)
- ii. Calculate the power dissipation in resistor  $R_1$ . (2 marks)
- iii. Calculate the power dissipation in resistor  $R_2$ . (2 marks)

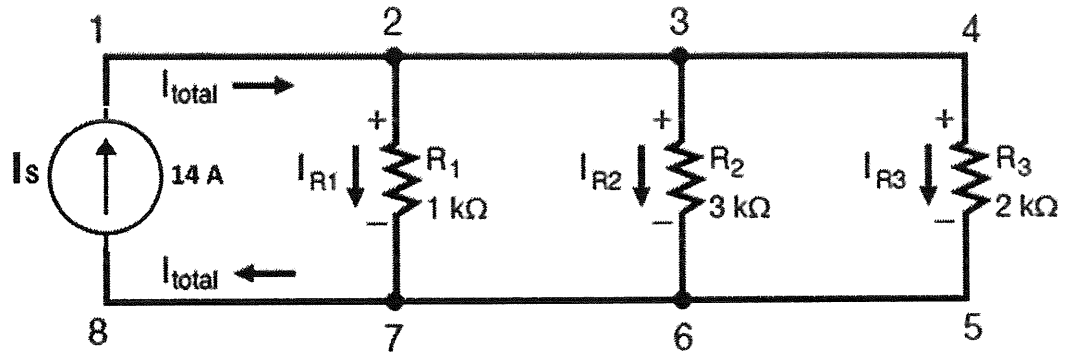
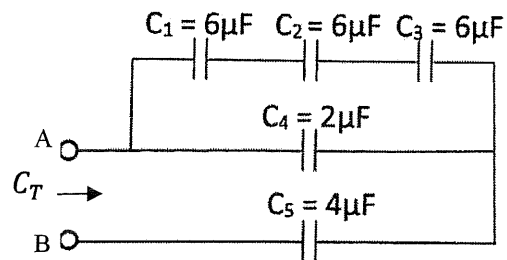


Figure 4

**QUESTION 3**

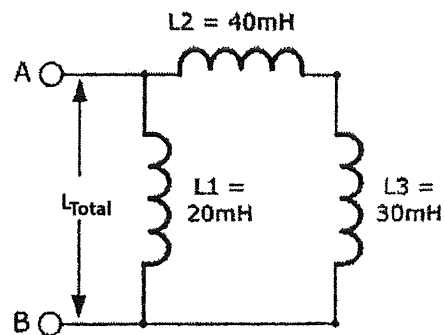
- a) When a capacitor is connected to a circuit with a DC supply, two processes called charging and discharging occur.
- Draw suitable circuit diagrams of the charging process of a capacitor.  
(4 marks)
  - Explain the charging process of a capacitor based on each diagram.  
(6 marks)
- b) Determine the total capacitance,  $C_T$  for the circuit in **Figure 5**.

**Figure 5**

(4 marks)

**QUESTION 4**

- a) An inductor is an electrical component that stores electrical energy in the magnetic field.
- Draw suitable diagrams of the basic operation of an inductor. (2 marks)
  - Describe the basic operation of an inductor. (8 marks)
- b) Determine the total inductance,  $L_{Total}$  for the circuit in **Figure 6**.

**Figure 6**

(4 marks)










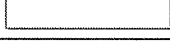


-----End of Questions-----

## APPENDIX I

1.	Charge	$Q = \frac{\text{number of electrons}}{6.25 \times 10^{18} \text{ e/C}}$
2.	Voltage	$V = \frac{W(\text{Joules})}{Q(\text{Coulombs})}$
3.	Current	$I = \frac{Q}{t}$
4.	Resistor value	$= AB \times 10^C \pm \%D \Omega$
5.	Ohm's Law	$V = IR$
6.	Power	$P = VI = I^2R = \frac{V^2}{R}$
7.	Series Capacitor	$C_T = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}}$
8.	Parallel Resistor	$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}$
9.	Parallel Inductor	$L_T = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}}$
10.	Voltage Divider	$V_x = \frac{R_x}{R_T} V_S$
11.	Current Divider	$I_x = \frac{R_T}{R_x} I_T$
		Where $R_T = R_1    R_2    \dots    R_n$

**APPENDIX II**

**The color code of resistors**

	Color	Digit	Multiplier	Tolerance	
<b>Resistance value, first three bands:</b> First band- 1st digit Second band- 2nd digit *Third band- multiplier (number of zeros following the 2nd digit)		Black	0	$10^0$	
		Brown	1	$10^1$	1% (five band)
		Red	2	$10^2$	2% (five band)
		Orange	3	$10^3$	
		Yellow	4	$10^4$	
		Green	5	$10^5$	
		Blue	6	$10^6$	
		Violet	7	$10^7$	
		Gray	8	$10^8$	
		White	9	$10^9$	
<b>Fourth band- tolerance</b>		Gold	$\pm 5\%$	$10^{-1}$	5% (four band)
		Silver	$\pm 10\%$	$10^{-2}$	10% (four band)
		No band	$\pm 20\%$		

\* For resistance values less than  $10\Omega$ , the third band is either gold or silver. Gold is for a multiplier of 0.1 and silver is for a multiplier of 0.01.

