

**UNIVERSITY COLLEGE TATI (UC TATI)****FINAL EXAMINATION QUESTION BOOKLET**

COURSE CODE	: BMT 1023
COURSE	: ELECTRICAL & ELECTRONICS TECHNOLOGY
SEMESTER / SESSION	: 01 - 2023/2024
DURATION	: 3 HOURS

**Instructions:**


1. This booklet contains **4** questions. Answer **ALL**.
2. All answers should be written in the answer booklet.
3. Write legibly and draw sketches wherever required.
4. If in doubt, raise your hand and ask the invigilator.

**DO NOT OPEN THIS BOOKLET UNTIL YOU ARE TOLD TO DO SO**

**THIS BOOKLET CONTAINS 7 PRINTED PAGES INCLUDING COVER PAGE**


**QUESTION 1**

- a) When a capacitor is connected to a circuit with a DC supply, two processes called charging and discharging occur.
- Draw suitable circuit diagrams of the charging process of a capacitor. (4 marks)
  - Explain the charging process of a capacitor based on each diagram. (6 marks)
- b) Based on the capacitor circuit as shown in **Figure 1**:

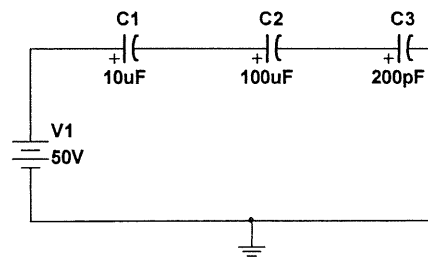**Figure 1**

- State the type of circuit arrangement. (1 mark)
  - Determine the total capacitance of the circuit. (3 marks)
- c) An inductor is an electrical component that stores electrical energy in the magnetic field.
- Draw suitable diagrams of the basic operation of an inductor. (2 marks)
  - Describe the basic operation of an inductor. (8 marks)

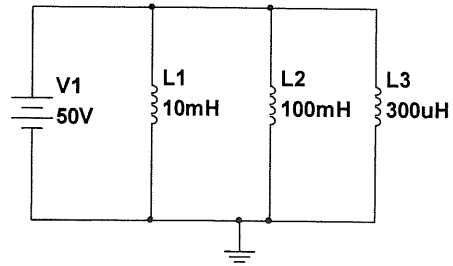d) Based on the inductor circuit as shown in **Figure 2**:

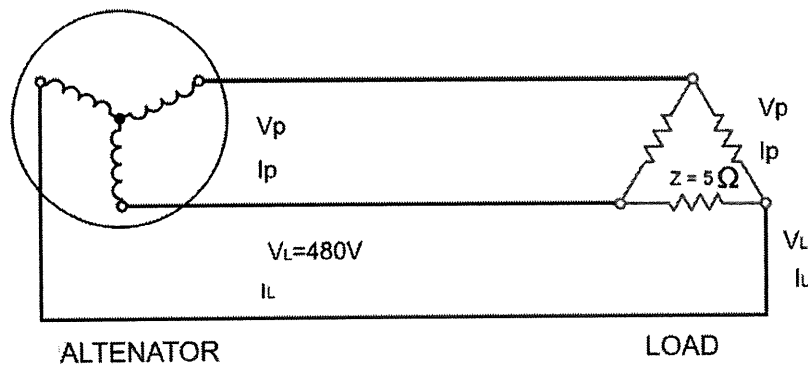


**Figure 2**

- i) State the type of circuit arrangement. (1 mark)
- ii) Determine the total inductance of the circuit. (3 marks)


**QUESTION 2**

- a) Explain six (6) advantages of three-phase AC power over single-phase AC power. (6 marks)
- b) A balanced three-phase resistive load having an impedance  $Z = 5 \Omega$  in each phase is supplied from 480 V, balanced three-phase alternator, as shown in **Figure 3**:

**Figure 3**

- i) State the connection of the supply. (1 mark)
- ii) State the connection of the load. (1 mark)
- iii) Determine the value for the phase current of the load,  $I_{P(LOAD)}$ . (3 marks)
- iv) Determine the value for the load current of the load,  $I_{L(LOAD)}$ . (3 marks)
- c) Discuss the properties of N-type semiconductors. (7 marks)

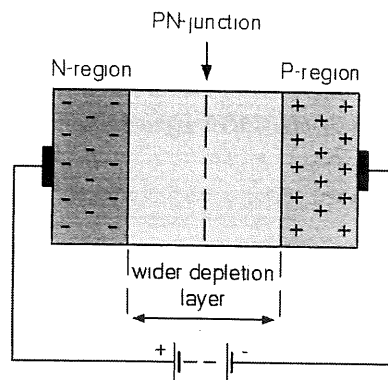d) Based on the p-n junction diode circuit as shown in **Figure 4**:

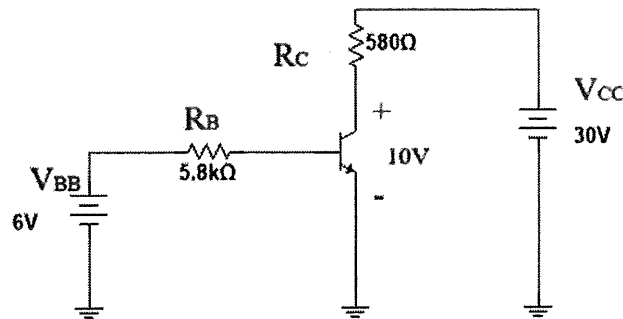


**Figure 4**

- i) State the type of diode biasing. (1 mark)
- ii) Describe the bias characteristics of the p-n junction diode. (6 marks)

**QUESTION 3**

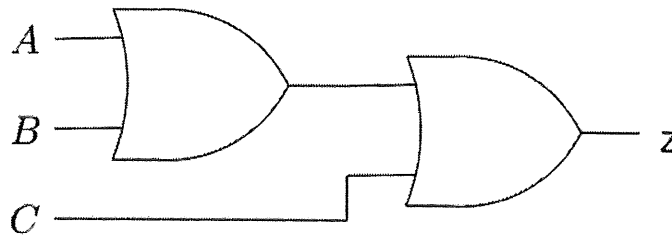
- a) Describe the free electron behavior of an NPN BJT using a suitable diagram and description. (7 marks)
- b) Based on the NPN BJT circuit as shown in **Figure 5**:

**Figure 5**

- i) State the biasing of the BE junction. (1 mark)
- ii) Determine the base current,  $I_B$  of the circuit. (3 marks)
- iii) Determine the collector current,  $I_C$  of the circuit. (3 marks)
- c) List four (4) advantages of the digital system. (4 marks)
- d) Convert the binary number  $110011_2$  to its decimal number equivalent using the sum of weight method. (3 marks)
- e) Convert the decimal number  $60_{10}$  to its binary number equivalent using the repetitive division method. (3 marks)


**QUESTION 4**

a) Based on the digital circuit as shown in **Figure 6**:

**Figure 6**

- i) Name the logic gate used in the circuit. (1 mark)
- ii) Determine the Boolean expression of the circuit. (2 marks)
- iii) Determine the complete truth table of the circuit. (8 marks)

b) Based on the digital circuit as shown in **Figure 7**:

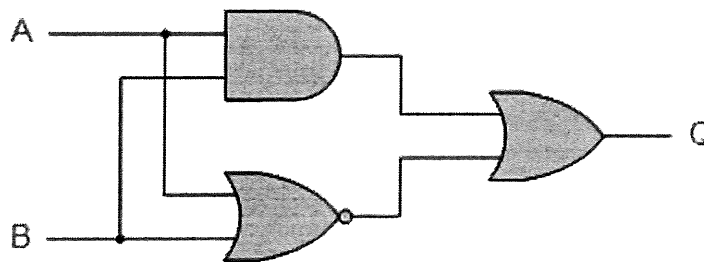**Figure 7**

- i) Name the logic gates used in the circuit. (3 marks)
- ii) Determine the Boolean expression of the circuit. (2 marks)
- iii) Determine the complete truth table of the circuit. (4 marks)

-----End of Questions-----

